

# Analog IC Design: Course Project

*A low-power low-noise CMOS amplifier for neural recording applications*

Jampana Koundinya Varma

2021112022

There is a need among scientists and clinicians for low-noise low-power bio-signal amplifiers capable of amplifying signals in the millihertz-to-kilohertz range while rejecting large dc offsets generated at the electrode–tissue interface. The advent of fully implantable multielectrode arrays has created the need for fully integrated micropower amplifiers.

## 1. Design Specifications


We are given to design the low noise low power neural amplifier (Fig. 1 in the paper) using the OTA topology (Fig. 4 in the paper) given in the following research paper: R. R. Harrison and C. Charles, *A low-power low-noise CMOS amplifier for neural recording applications*.

The specifications of the design are as follows:

- DC gain  $\geq 60\text{dB}$
- -3dB bandwidth  $\geq 10\text{kHz}$
- Input referred noise  $\leq 2\mu\text{V}_{\text{rms}}$
- CMRR  $\geq 100\text{dB}$
- Noise Efficiency Factor (NEF)  $\leq 4$
- DC power consumption  $\leq 30\mu\text{A}$
- Supply Voltage  $\leq 1.8\text{V}$

## 2. Hand Calculations

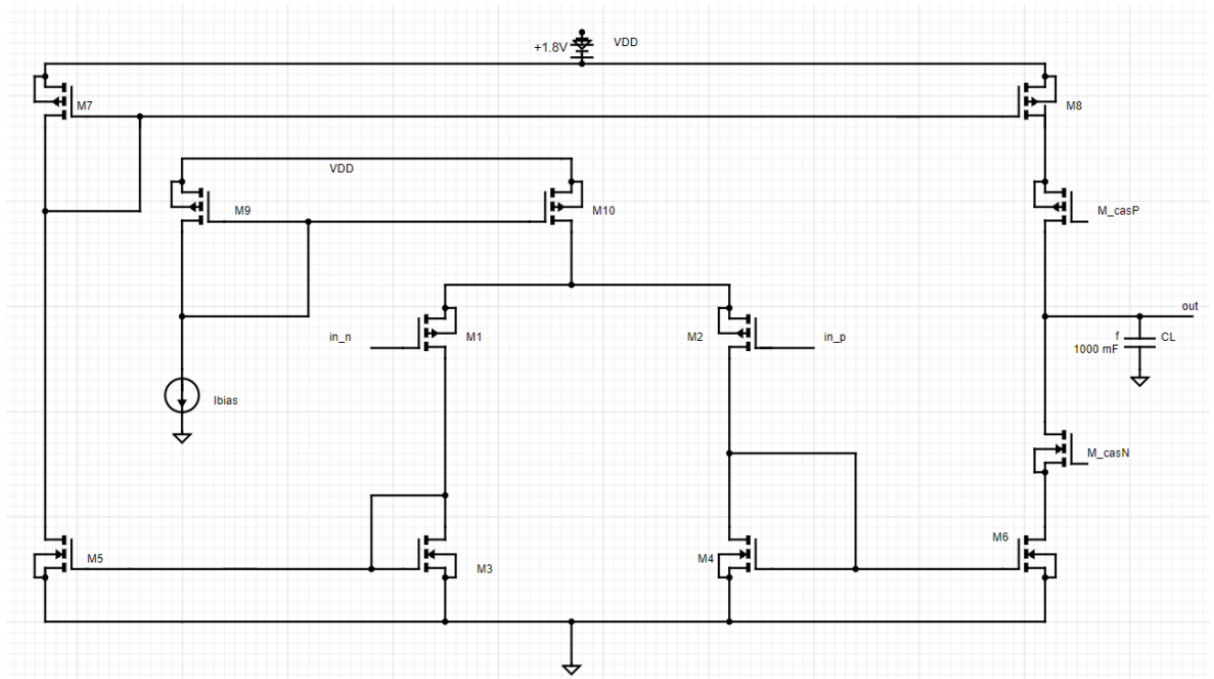- a) OTA schematic using circuit-diagram.org is as follows including labelled transistors, resistors, and capacitors.



b) The step-by-step design procedure and calculations are as follows.

Given

$$I_{DC} \leq 30 \mu A$$

$$V_{DD} = -V_{CS} = \pm 1.8 V$$

Firstly we calculate the gain expression for this OTA.

The output resistance  $R_{out}$  is given by

$$g_{m1} r_{o1}^2 \parallel g_{m2} r_{o2}^2 \quad \because g_{m1} = g_{m2}$$

$$\approx \frac{g_{m1} r_{o1}^2}{2}$$

Now we find the incremental current expression

Referring to the circuit schematic

above we have, the incremental current as follows considering  $V_-$  at  $\downarrow$  and  $V_+$  at  $\uparrow$

$$\begin{array}{ll} \text{for } M_1: g_{m1} V_{in} \downarrow & M_5: (g_{m1} V_{in}) \left( \frac{g_{m5}}{g_{m2}} \right) \downarrow \\ M_2: g_{m1} V_{in} \uparrow & M_6: (g_{m1} V_{in}) \left( \frac{g_{m6}}{g_{m4}} \right) \uparrow \\ M_3: g_{m1} V_{in} \downarrow & M_7: (g_{m1} V_{in}) \left( \frac{g_{m7}}{g_{m3}} \right) \left( \frac{g_{m8}}{g_{m1}} \right) \downarrow \\ M_4: g_{m1} V_{in} \uparrow & \quad \quad \quad (-g_{m7} g_{m8}) \end{array}$$

$$\text{So the incremental current} = g_{m1} V_{in} \left[ \frac{g_{m8}}{g_{m1}} + \frac{g_{m6}}{g_{m4}} \right]$$

So the differential gain is

$$A = g_{m1} \left( \frac{g_{m8}}{g_{m1}} + \frac{g_{m6}}{g_{m4}} \right) \left( \frac{g_{m1} r_{o1}^2}{2} \right)$$

As  $g_{m1} \cdot g_{m4} \geq 10^{-11}$

$$g_{m1} \geq \frac{10^{-11}}{42 \times 10^{-6}}$$

$$g_{m1} \geq 0.25 \mu$$

Given that input referred noise  $\leq 2 \mu \text{ Vrms}$

Firstly the  $\overline{V_{noise}^2} = 4KT \cdot (g_{m1} + g_{m2} + g_{m3} + g_{m4} + g_{m5} + g_{m6} + g_{m7} + g_{m8})$

as  $\overline{V_{in}^2} = \frac{\overline{V_{noise}^2}}{A^2}$

$$= \frac{8KT \cdot 16}{g_{m1}} \left[ 1 + \frac{2g_{m3}}{g_{m1}} + \frac{g_{m7}}{g_{m1}} \right]$$

as  $\gamma = \frac{4}{2}$ ; we have-

$$\sqrt{\frac{16KT}{3g_{m1}} \left[ 1 + \frac{2g_{m3}}{g_{m1}} + \frac{g_{m7}}{g_{m1}} \right]} \leq 2 \mu \text{ Vrms}$$

Now from NBF:

$$\overline{V_{in, rms}^2} \cdot \frac{2(24\mu)}{\pi (26 \times 10^{-3}) (4 \times 4.4 \times 10^{-4}) \times 10^4} \leq 16$$

$$V_{in, rms} \leq 2.1 \mu$$

$$\frac{16KT}{3g_{m1}} \left[ 1 + \frac{2g_{m3}}{g_{m1}} \right] \leq 4 \times 10^{-12}$$


$$1 + \frac{2g_{m3}}{g_{m1}} \leq 7.66 \times 10^3$$

$$3g_{m3} \leq 320 \times 10^{-3}$$

$$g_{m3} \leq 100 \text{ m}$$

### 3. OTA Simulations

#### a. Circuit Schematic

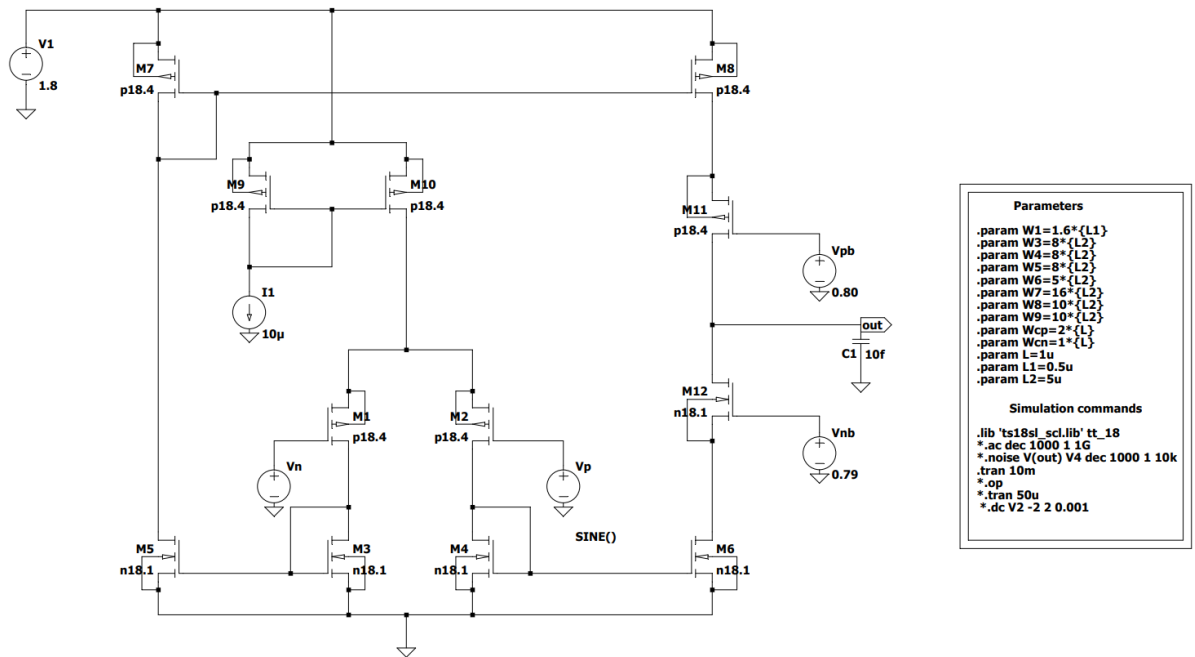


#### b. Design Parameters

|                                 |           |
|---------------------------------|-----------|
| <b>Current I<sub>bias</sub></b> | 10μ       |
| <b>Load Capacitance</b>         | 10fF      |
| <b>M1, M2</b>                   | 0.8μ/0.5μ |
| <b>M3, M4, M5</b>               | 40μ/5μ    |
| <b>M6</b>                       | 32μ/5μ    |
| <b>M7</b>                       | 80μ/5μ    |
| <b>M8</b>                       | 50μ/5μ    |
| <b>M9, M10</b>                  | 50μ/5μ    |
| <b>Mcasep</b>                   | 2μ/1μ     |
| <b>Mcasen</b>                   | 1μ/1μ     |
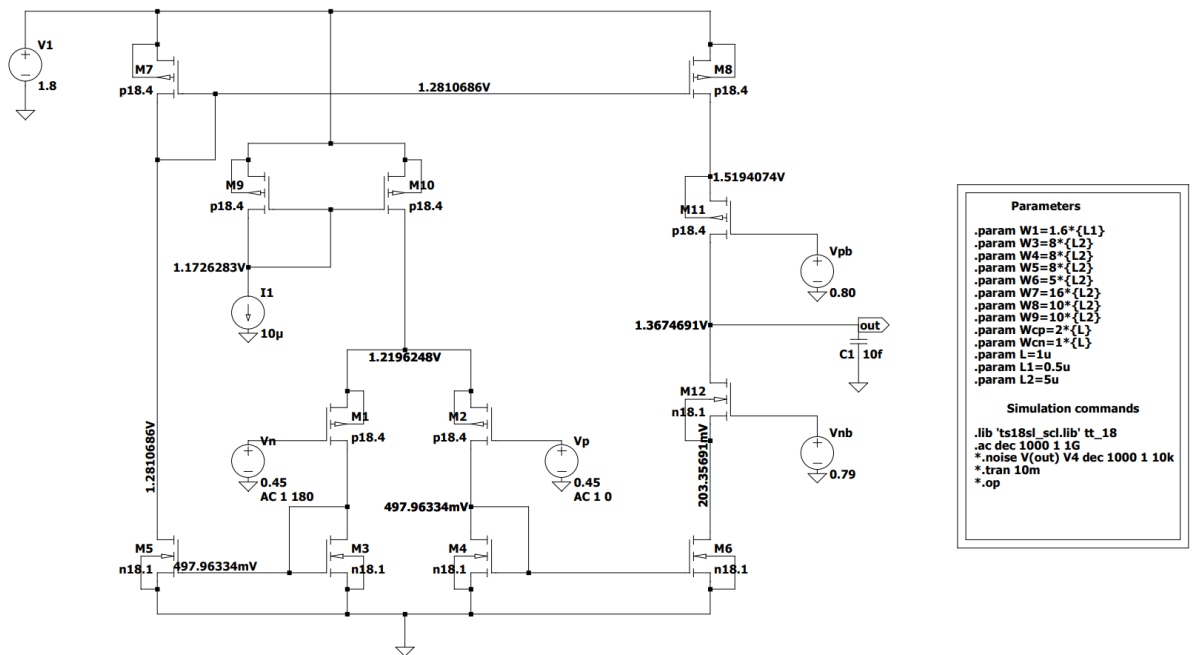
#### c. Operating Point

The Operating Point analysis of the OTA is as follows, where the DC voltage have been annotated at each node as instructed. We observe that all the transistors are biased to be in saturation.



The obtained values for Operating Point analysis are as follows.

```

--- Operating Point ---
V(n008) :      1.21962      voltage
V(n011) :      0.45        voltage
V(n013) :      0.497963    voltage
V(n009) :      0.203357    voltage
V(n014) :      0.497963    voltage
V(n001) :      1.8         voltage
V(n002) :      1.28107     voltage
V(n003) :      1.51941     voltage
V(n006) :      1.17263     voltage
V(out) :      1.36747      voltage
V(n010) :      0.79        voltage
V(n007) :      0.8         voltage
V(n012) :      0.45        voltage

```

|          |           |           |           |           |           |
|----------|-----------|-----------|-----------|-----------|-----------|
| Name:    | m12       | m4        | m5        | m6        | m3        |
| Model:   | n18.1     | n18.1     | n18.1     | n18.1     | n18.1     |
| Id:      | 3.13e-06  | 5.00e-06  | 5.02e-06  | 3.13e-06  | 5.00e-06  |
| Vgs:     | 5.87e-01  | 4.98e-01  | 4.98e-01  | 4.98e-01  | 4.98e-01  |
| Vds:     | 1.16e+00  | 4.98e-01  | 1.28e+00  | 2.03e-01  | 4.98e-01  |
| Vbs:     | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  |
| Vth:     | 3.99e-01  | 3.70e-01  | 3.70e-01  | 3.70e-01  | 3.70e-01  |
| Vdsat:   | 1.90e-01  | 1.18e-01  | 1.18e-01  | 1.18e-01  | 1.18e-01  |
| Gm:      | 3.21e-05  | 9.45e-05  | 9.51e-05  | 5.87e-05  | 9.45e-05  |
| Gds:     | 6.90e-08  | 5.81e-08  | 2.32e-08  | 5.10e-07  | 5.81e-08  |
| Gmb:     | 6.06e-06  | 1.74e-05  | 1.75e-05  | 1.08e-05  | 1.74e-05  |
| Cbd:     | 2.44e-15  | 4.86e-13  | 3.99e-13  | 3.39e-13  | 4.86e-13  |
| Cbs:     | 3.50e-15  | 5.98e-13  | 5.98e-13  | 3.74e-13  | 5.98e-13  |
| Cgsov:   | 2.20e-16  | 8.80e-15  | 8.80e-15  | 5.50e-15  | 8.80e-15  |
| Cgdov:   | 2.20e-16  | 8.80e-15  | 8.80e-15  | 5.50e-15  | 8.80e-15  |
| Cgbov:   | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  |
| dQgdVgb: | 6.46e-15  | 1.09e-12  | 1.09e-12  | 7.15e-13  | 1.09e-12  |
| dQgdVdb: | -2.21e-16 | -1.10e-14 | -8.88e-15 | -4.88e-14 | -1.10e-14 |
| dQgdVsb: | -5.32e-15 | -8.73e-13 | -8.72e-13 | -5.43e-13 | -8.73e-13 |
| dQddVgb: | -2.73e-15 | -4.66e-13 | -4.64e-13 | -3.13e-13 | -4.66e-13 |
| dQddVdb: | 2.66e-15  | 4.97e-13  | 4.08e-13  | 3.74e-13  | 4.97e-13  |
| dQddVsb: | 3.04e-15  | 5.53e-13  | 5.52e-13  | 3.44e-13  | 5.53e-13  |
| dQbdVgb: | -1.00e-15 | -1.61e-13 | -1.62e-13 | -8.93e-14 | -1.61e-13 |
| dQbdVdb: | -2.44e-15 | -4.87e-13 | -3.99e-13 | -3.54e-13 | -4.87e-13 |
| dQbdVsb: | -4.49e-15 | -8.39e-13 | -8.38e-13 | -5.23e-13 | -8.39e-13 |

|          |           |           |           |           |           |
|----------|-----------|-----------|-----------|-----------|-----------|
| Name:    | m11       | m2        | m7        | m9        | m10       |
| Model:   | p18.4     | p18.4     | p18.4     | p18.4     | p18.4     |
| Id:      | 3.13e-06  | 5.00e-06  | 5.02e-06  | 1.00e-05  | 1.00e-05  |
| Vgs:     | -5.67e-01 | -4.80e-02 | 0.00e+00  | 0.00e+00  | -4.70e-02 |
| Vds:     | 1.52e-01  | 7.22e-01  | 5.19e-01  | 6.27e-01  | 5.80e-01  |
| Vbs:     | 1.52e-01  | 7.22e-01  | 5.19e-01  | 6.27e-01  | 5.80e-01  |
| Vth:     | -4.12e-01 | -4.18e-01 | -4.05e-01 | -4.05e-01 | -4.05e-01 |
| Vdsat:   | -2.66e-01 | -2.99e-01 | -1.20e-01 | -2.00e-01 | -2.00e-01 |
| Gm:      | 1.39e-05  | 2.58e-05  | 6.78e-05  | 8.33e-05  | 8.32e-05  |
| Gds:     | 1.23e-05  | 4.21e-07  | 5.44e-08  | 9.85e-08  | 1.12e-07  |
| Gmb:     | 4.41e-06  | 7.53e-06  | 2.08e-05  | 2.57e-05  | 2.57e-05  |
| Cbd:     | 6.05e-15  | 1.49e-15  | 1.01e-12  | 6.29e-13  | 6.29e-13  |
| Cbs:     | 5.70e-15  | 1.21e-15  | 8.37e-13  | 5.09e-13  | 5.15e-13  |
| Cgsov:   | 5.20e-16  | 2.08e-16  | 2.08e-14  | 1.30e-14  | 1.30e-14  |
| Cgdov:   | 5.20e-16  | 2.08e-16  | 2.08e-14  | 1.30e-14  | 1.30e-14  |
| Cgbov:   | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  | 0.00e+00  |
| dQgdVgb: | 1.60e-14  | 3.11e-15  | 2.25e-12  | 1.51e-12  | 1.51e-12  |
| dQgdVdb: | -4.11e-15 | -2.09e-16 | -2.35e-14 | -1.48e-14 | -1.54e-14 |
| dQgdVsb: | -1.08e-14 | -2.59e-15 | -1.81e-12 | -1.28e-12 | -1.28e-12 |
| dQddVgb: | -7.45e-15 | -1.29e-15 | -9.01e-13 | -6.30e-13 | -6.31e-13 |
| dQddVdb: | 9.65e-15  | 1.70e-15  | 1.03e-12  | 6.44e-13  | 6.44e-13  |
| dQddVsb: | 5.97e-15  | 1.41e-15  | 1.17e-12  | 8.14e-13  | 8.15e-13  |
| dQbdVgb: | -1.10e-15 | -5.30e-16 | -4.44e-13 | -2.53e-13 | -2.53e-13 |
| dQbdVdb: | -8.62e-15 | -1.50e-15 | -1.01e-12 | -6.30e-13 | -6.30e-13 |
| dQbdVsb: | -7.40e-15 | -1.65e-15 | -1.38e-12 | -8.70e-13 | -8.76e-13 |




|          |           |           |
|----------|-----------|-----------|
| Name:    | m8        | m1        |
| Model:   | p18.4     | p18.4     |
| Id:      | 3.13e-06  | 5.00e-06  |
| Vgs:     | -2.38e-01 | -4.80e-02 |
| Vds:     | 2.81e-01  | 7.22e-01  |
| Vbs:     | 2.81e-01  | 7.22e-01  |
| Vth:     | -4.05e-01 | -4.18e-01 |
| Vdsat:   | -1.20e-01 | -2.99e-01 |
| Gm:      | 4.22e-05  | 2.58e-05  |
| Gds:     | 1.44e-07  | 4.21e-07  |
| Gmb:     | 1.30e-05  | 7.53e-06  |
| Cbd:     | 6.29e-13  | 1.49e-15  |
| Cbs:     | 5.63e-13  | 1.21e-15  |
| Cgsov:   | 1.30e-14  | 2.08e-16  |
| Cgdov:   | 1.30e-14  | 2.08e-16  |
| Cgbov:   | 0.00e+00  | 0.00e+00  |
| dQgdVgb: | 1.42e-12  | 3.11e-15  |
| dQgdVdb: | -2.87e-14 | -2.09e-16 |
| dQgdVsb: | -1.13e-12 | -2.59e-15 |
| dQddVgb: | -5.73e-13 | -1.29e-15 |
| dQddVdb: | 6.54e-13  | 1.70e-15  |
| dQddVsb: | 7.30e-13  | 1.41e-15  |
| dQbdVgb: | -2.71e-13 | -5.30e-16 |
| dQbdVdb: | -6.37e-13 | -1.50e-15 |
| dQbdVsb: | -9.05e-13 | -1.65e-15 |


From the operating points obtained, it can be seen that all MOSFETs are in saturation mode. The current is mirrored as per the requirements. Hence, the devices are biased properly.

#### d. Stability Analysis

- The DC gain is observed to be 53.18dB

 

 - The Unity gain frequency is observed to be 7.11MHz



- The phase margin is observed to be almost 37 degrees from the above graph.

#### e. Slew Rate

After giving a positive step from 0 to 1.8V with a rise time of 100 ps in unity gain feedback mode.

The slew rate =  $522.05388\text{ns}/1.8 = 0.29\text{MV/s} = 0.29\text{V}/\mu\text{s}$ .



#### f. Settling Time

The settling time for 2% accuracy is when we apply the same step input as above and finding the settling time which is at  $V=1.764\text{V}$


From the following plot we observe that the settling time is 194.19692ns.






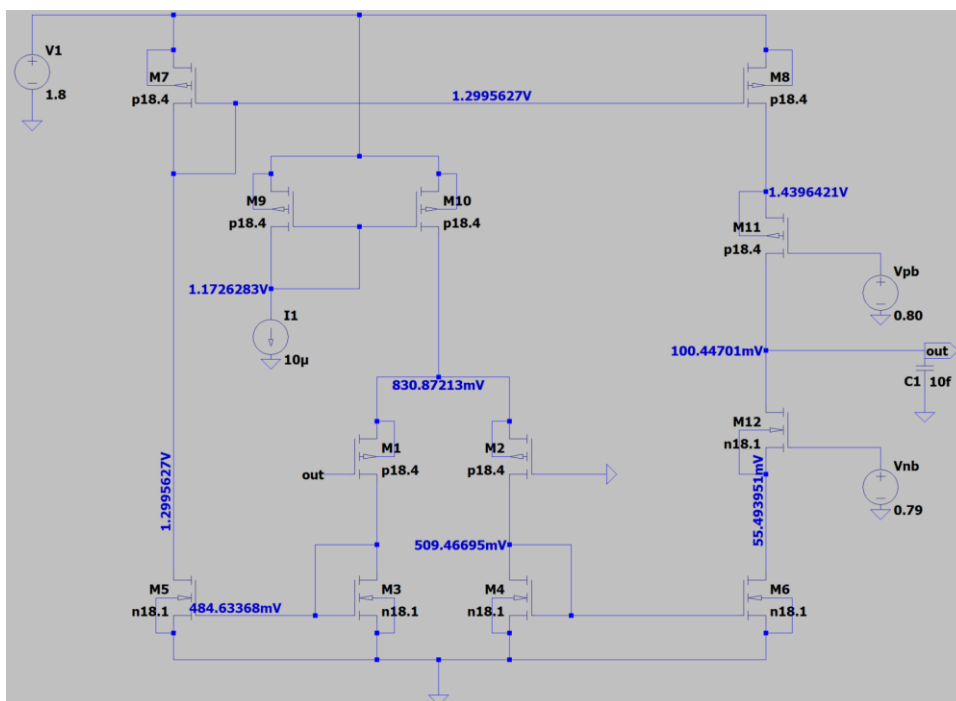g. Systematic Offset

The systematic offset obtained after following given steps is 100.44mV





 


From the above obtained plot, we have

Common mode gain ( $A_c$ ) = -49.9dB

Differential mode gain ( $A_d$ ) = 53.18dB

Now, the Common Mode Rejection Ratio (CMRR) =  $A_d(\text{dB}) - A_c(\text{dB}) = 103.08\text{dB}$

j. PSRR

 


The obtained PSRR from the above figure is hence  $53.18\text{dB} - (-59.99\text{dB}) = 113.18\text{dB}$

k. ICMR

From the below graph the ICMR obtained after following the given steps is

$$0.252\text{mV} < \text{ICMR} < 1.67\text{V}$$

So it has a range around 1.42V.

 


### l. Closed Loop Gain

The -3dB bandwidth was observed around 2.1Mhz for the closed loop gain.


 
### m. Closed Loop Transient Analysis


The closed loop transient analysis for input of around 100mV is as follows




#### n. Power Consumption


Total Current drawn from the source is  $10+10+5+4 = 29\mu\text{A}$ , so the total DC power consumed is  $1.8(\text{VDD})$  times  $29\mu\text{A}$ (I drawn), which is  $52.2\mu\text{W}$ .

**Pseudo Resistor** is shown as follows

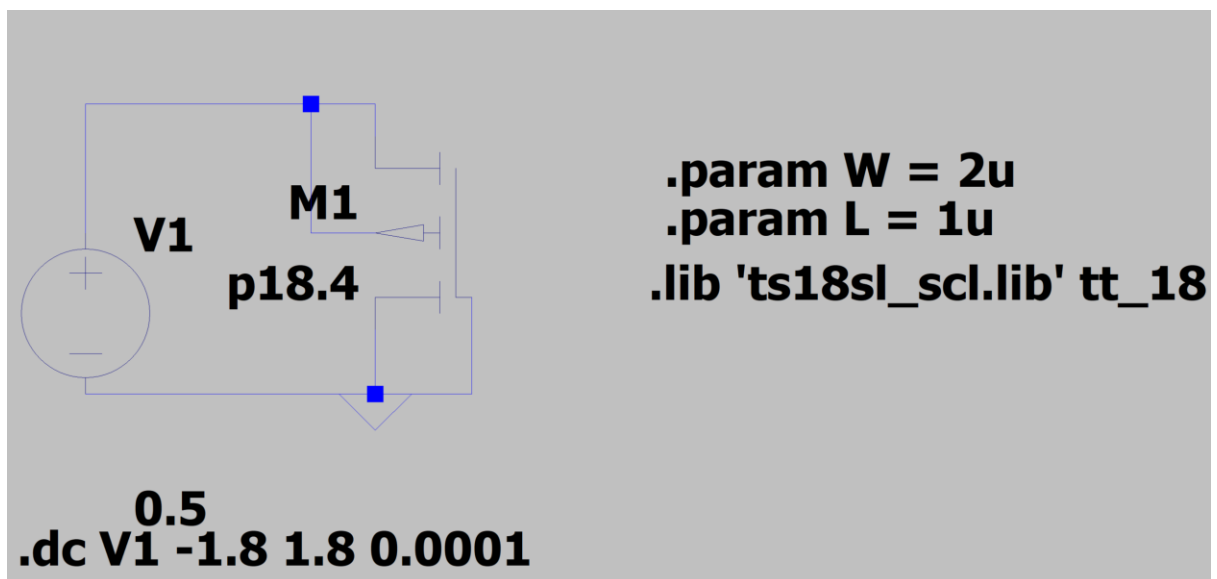

 

 
Above is the obtained I-V diagram for the pseudo-resistor. And the obtained incremental resistance vs incremental voltage is plotted below, from where we observe that the maximum incremental resistance is  $15.7\text{G}\Omega$ .


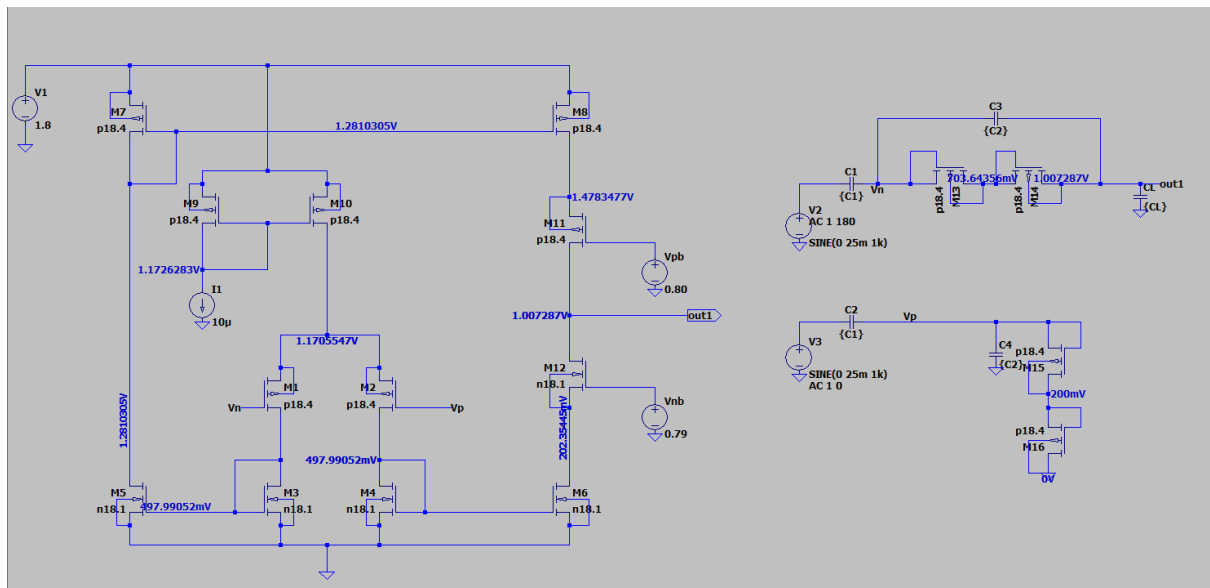
## Neural Amplifier

The values of  $C_1$ ,  $C_2$  and the sizing of the pseudo resistor is taken from the reference paper which gives  $C_1$  as  $0.2\text{nF}$ ,  $C_2$  as  $200\text{fF}$  and  $W/L$  to be  $4\mu/4\mu$ . The values can also be calculated from the input and output resistances with the frequency to be less than the bandwidth at both input and output nodes. The final circuit is as follows.





AC Response